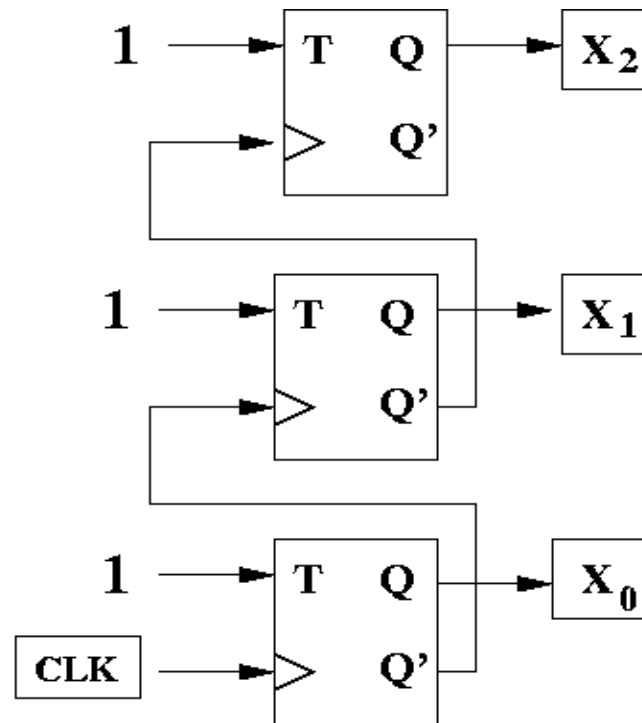


Finite state machines: counter

Asynchronous counter: flip-flops driven by different clocks

Clock period of each successive flip-flop is 2 times previous one
power of 2 times the first clock



Finite state machines: counter

Use FSM to implement a synchronous counter

2-bit (mod 4) counter

starts at 00

counts up to 11

resets to 00 after 11

Finite state machine

state (q): 2 bits, initially 00

output (z): same as state

input

x = 0: same state


x = 1: increment

Usage

Keeping track of number of bits sent

Program counter (PC)

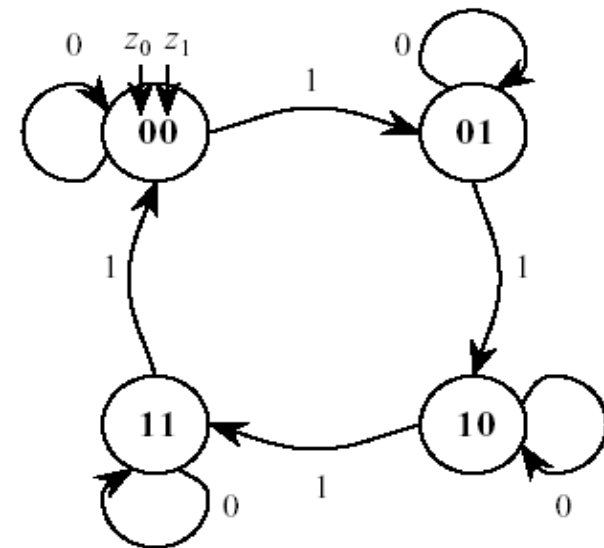Increments each clock cycle to point to next instruction




Principles of Computer Architecture by M. Murdocca and V. Heuring

Finite state machines: counter


q_1	q_0	x
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

1a. State transition table inputs

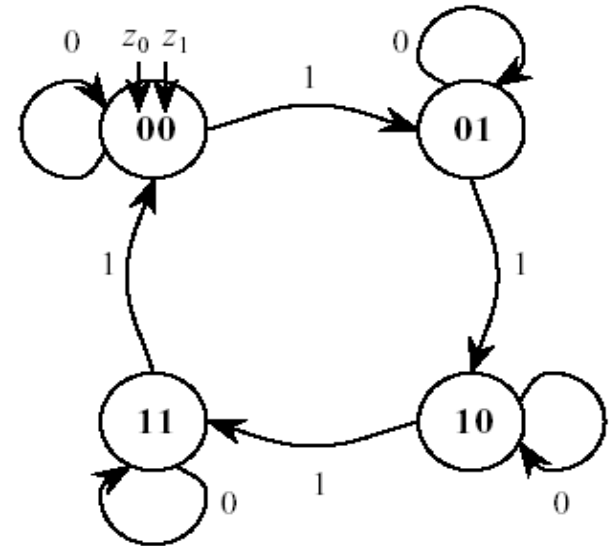

Finite state machines: counter

q_1	q_0	x	q_1^+	q_0^+
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

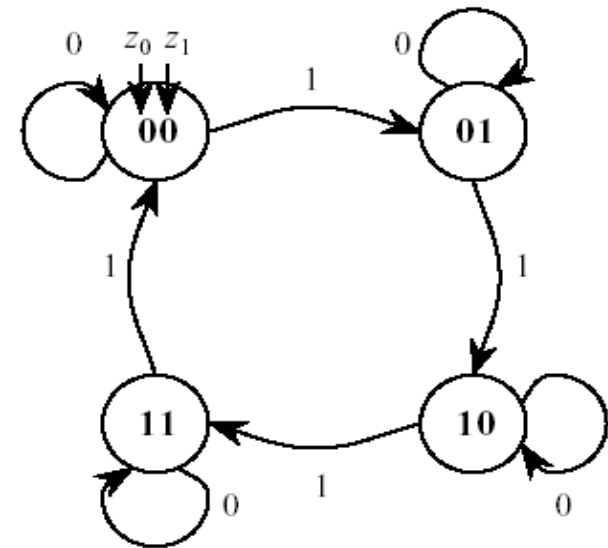


1b. New state

input 0: no change

input 1: increment

Finite state machines: counter

q_1	q_0	x	q_1^+	q_0^+	z_1	z_0
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	0	1	0	1
0	1	1	1	0	0	1
1	0	0	1	0	1	0
1	0	1	1	1	1	0
1	1	0	1	1	1	1
1	1	1	0	0	1	1

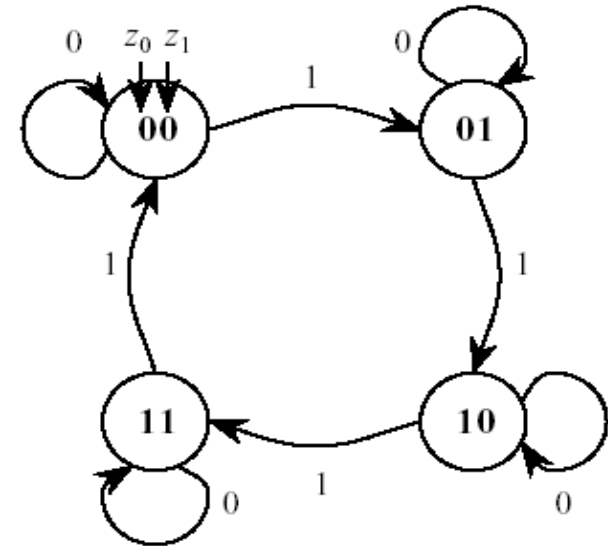

Principles of Computer Architecture by M. Murdocca and V. Heuring


1c. Output: same as current state label

Note that the figure reverses our usual definition of the output bits

Finite state machines: counter

q_1	q_0	x	q_1^+	q_0^+	z_1	z_0	D_1	D_0
0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	1
0	1	0	0	1	0	1	0	1
0	1	1	1	0	0	1	1	0
1	0	0	1	0	1	0	1	0
1	0	1	1	1	1	0	1	1
1	1	0	1	1	1	1	1	1
1	1	1	0	0	1	1	0	0

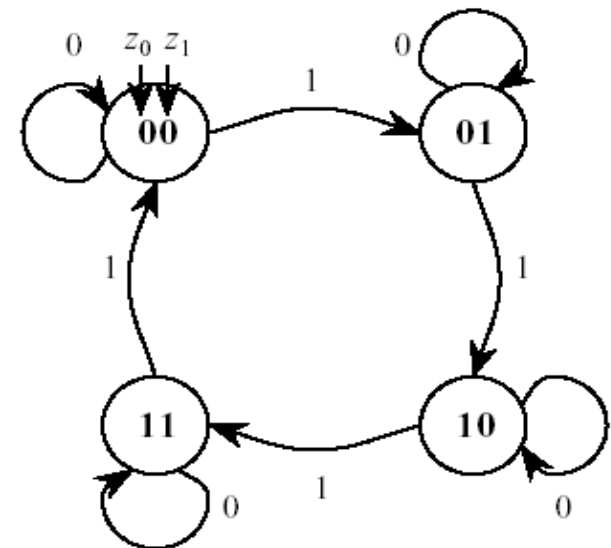- Pick flip-flops: both D
- Use excitation tables to get values for D
(copy columns for next state)



Finite state machines: counter

Input			Next		Output				ROM	
q_1	q_0	x	q_1^+	q_0^+	z_1	z_0	D_1	D_0	Address	Data
0	0	0	0	0	0	0	0	0	000	0000
0	0	1	0	1	0	0	0	1	001	0001
0	1	0	0	1	0	1	0	1	010	0101
0	1	1	1	0	0	1	1	0	011	0110
1	0	0	1	0	1	0	1	0	100	1010
1	0	1	1	1	1	0	1	1	101	1011
1	1	0	1	1	1	1	1	1	110	1111
1	1	1	0	0	1	1	0	0	111	1100

4. Draw circuit: ROM

address: q_1q_0x

data: $z_1z_0D_1D_0$

Finite state machines: counter

Input			Next		Output				Minterms
q_1	q_0	x	q_1^+	q_0^+	z_1	z_0	D_1	D_0	z_1
0	0	0	0	0	0	0	0	0	
0	0	1	0	1	0	0	0	1	
0	1	0	0	1	0	1	0	1	
0	1	1	1	0	0	1	1	0	
1	0	0	1	0	1	0	1	0	$q_1 \backslash q_0 \backslash x$
1	0	1	1	1	1	0	1	1	$q_1 \backslash q_0 x$
1	1	0	1	1	1	1	1	1	$q_1 q_0 \backslash x$
1	1	1	0	0	1	1	0	0	$q_1 q_0 x$

4. Draw circuit: gates

Minterms

$$z_1 = q_1 \backslash q_0 \backslash x + q_1 \backslash q_0 x + q_1 q_0 \backslash x + q_1 q_0 x$$

etc.

Simplified

$$z_1 = q_1$$

$$z_0 = q_0$$


$$D_1 = q_1 \backslash q_0 + q_0 (\backslash q_1 x + q_1 \backslash x)$$

$$D_0 = \backslash q_0 x + q_0 \backslash x$$

Finite state machines: 3-state counter

Note that it is not necessary to use all possible states for the counter

3-state counter: reset to 00 after 10

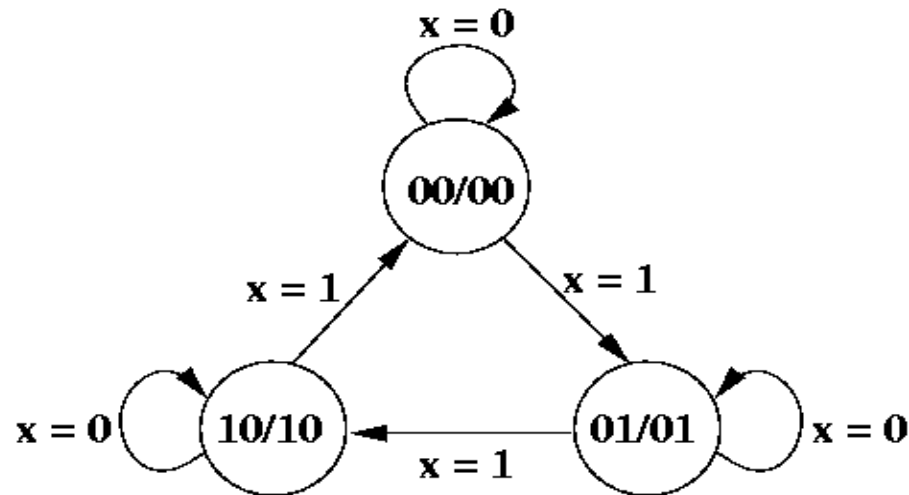


Changes:

Replace entries for state 11 in state transition table with "d"

Next state after state 10 is 00 with input 1

Finite state machines: 3-state counter

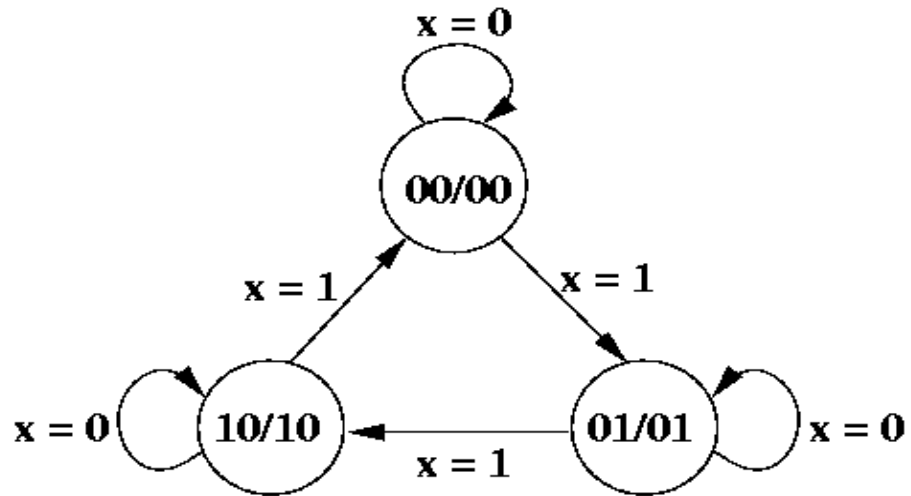

Input			Next		Output			
q_1	q_0	x	q_1^+	q_0^+	z_1	z_0	D_1	D_0
0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	1
0	1	0	0	1	0	1	0	1
0	1	1	1	0	0	1	1	0
1	0	0	1	0	1	0	1	0
1	0	1	0	0	1	0	0	0
1	1	0	d	d	d	d	d	d
1	1	1	d	d	d	d	d	d

Finite state machines: counter


Other possible counter variations

Use Mealy machine

Use input to reset

Input 0: increment

Input 1: reset

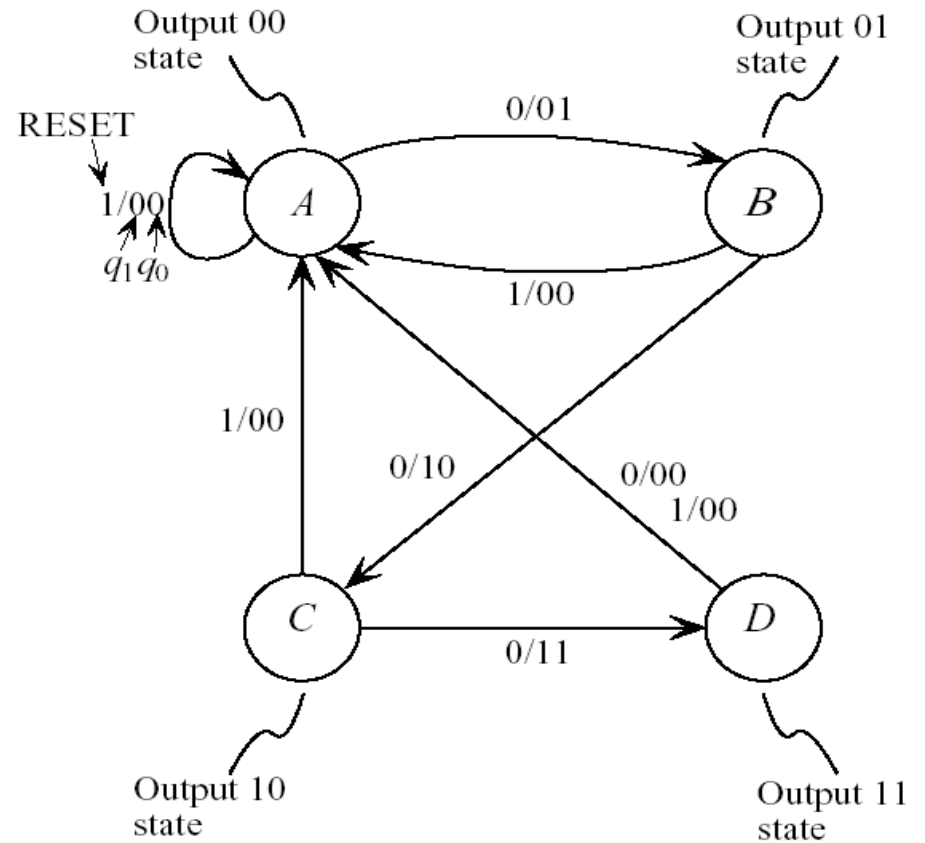

Finite state machines: counter

Other possible counter variations

Decrement

Input 0: hold

Input 1: decrement

Increment/decrement

Input 0: increment

Input 1: decrement

Additional inputs

Asynchronous clear: reset value immediately to 00

Enable/disable

When this input is 0, counter continues to output current value

When 1, perform normal operations

Additional output

Counter out

Normally 1, but 0 when maximum value is reached

What could this be used for?

(Think of a connection with enable)

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.